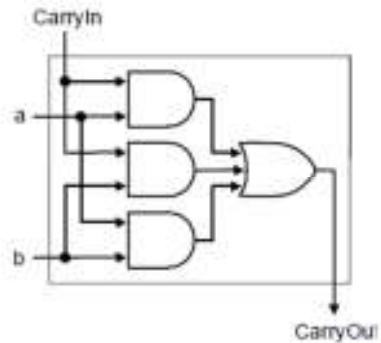


## Problem (4) B.30, Answer C

### Assumption:

1. a delay of gate is proportion to the number of fan-ins (inputs):  $kT$  ( $k=\text{fanin}$ )
2. 1bit full adder:  $\text{CarryOut} = 2T + 3T = 5T$ ,  $\text{Sum} = 3T$  ( $a \text{ xor } b \text{ xor } C$ )
3. Carry-Lookahead Unit implementation: a sum of products (**same as the textbook and lecture slides**)



a. 64bit ripple carry adder:  $c_{64} = 320T$  ( $5T \times 64$ ),  $\text{Sum}_{63} = 318T$  ( $c_{63} + 3T$ )

b. 64bit ripple carry adder using 4 bit carry-lookahead adder:  $c_{64} = 162T$ ,  $\text{Sum} = 163T$

**CLA4bit<sub>3,0</sub>**:  $c_4 = 12T$ ,  $\text{Sum}_{3,0} = \max(\text{Sum}_3, \text{Sum}_2, \text{Sum}_1, \text{Sum}_0) = \max(13T, 11T, 9T, 3T) = 13T$

The details of delay calculations follow:

**The delay of output = gate delay + the max delay among input signals**

$p_i = a * b = 2T$ ,  $g_i = a \text{ xor } b = 2T$  from each one bit adder

Carry-lookahead unit (CLU) generates  $c_1, c_2, c_3, c_4$

$$\begin{aligned} c_1 &= g_0 + p_0 * c_0 = 2T(\text{gate delay of 2-input or}) + \max(g_0, 2T(\text{gate delay of 2-input and}) + \max(p_0, c_0)) \\ &= 2T + \max(2T, 2T + \max(2T, 0T)) = 2T + \max(2T, 4T) = 2T + 4T = 6T \end{aligned}$$

$$c_2 = g_1 + p_1 * g_0 + p_1 * p_0 * c_0 = 3T + \max(g_1, p_1 * g_0, p_1 * p_0 * c_0) = 3T + \max(2T, 2T + 2T, 3T + 2T) = 3T + 5T = 8T$$

$$\begin{aligned} c_3 &= g_2 + p_2 * g_1 + p_2 * p_1 * g_0 + p_2 * p_1 * p_0 * c_0 = 4T + \max(g_2, p_2 * g_1, p_2 * p_1 * g_0, p_2 * p_1 * p_0 * c_0) \\ &= 4T + \max(2T, 2T + 2T, 3T + 2T, 4T + 2T) = 4T + \max(2T, 4T, 5T, 6T) = 10T \end{aligned}$$

$$\begin{aligned} c_4 &= g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0 + p_3 * p_2 * p_1 * p_0 * c_0 \\ &= 5T + \max(g_3, p_3 * g_2, p_3 * p_2 * g_1, p_3 * p_2 * p_1 * g_0, p_3 * p_2 * p_1 * p_0 * c_0) \\ &= 5T + \max(2T, 2T + 2T, 3T + 2T, 4T + 2T, 5T + 2T) = 5T + \max(2T, 4T, 5T, 6T, 7T) = 12T \end{aligned}$$

$\text{Sum} = 3T$  (gate delay of 3-input xor) +  $\max(A_i, B_i, C_i)$ , but  $A_i$  and  $B_i$  are always  $0T$ .

So,  $\text{Sum} = 3T + \text{the delay of } C_i$

$$\text{Sum}_0 = 3T + c_0 = 3T + 0T = 3T$$

$$\text{Sum}_1 = 3T + c_1 = 3T + 6T = 9T$$

$$\text{Sum}_2 = 3T + c_2 = 3T + 8T = 11T$$

$$\text{Sum}_3 = 3T + c_3 = 3T + 10T = 13T$$

**CLA4bit<sub>7,4</sub>:**  $c_8 = 22T$ ,  $\text{Sum}_{7,4} = \max(\text{Sum}_7, \text{Sum}_6, \text{Sum}_5, \text{Sum}_4) = \max(23T, 21T, 19T, 15T) = 23T$

$p_i = a * b = 2T$ ,  $g_i = a \text{ xor } b = 2T$  from each one bit adder

Carry-lookahead unit (CLU) generates  $c_5, c_6, c_7, c_8$

$$\begin{aligned} c_5 &= g_4 + p_4 * c_4 = 2T + \max(2T, 2T + \max(p_4, c_4)) = 2T + \max(2T, 2T + \max(2T, 12T)) = 2T + 14T = 16T \\ c_6 &= g_5 + p_5 * g_4 + p_5 * p_4 * c_4 = 3T + \max(g_5, p_5 * g_4, p_5 * p_4 * c_4) = 3T + \max(2T, 4T, 3T + \max(p_5, p_4, c_4)) \\ &= 3T + \max(2T, 4T, 3T + \max(2T, 2T, 12T)) = 3T + \max(2T, 4T, 15T) = 3T + 15T = 18T \\ c_7 &= g_6 + p_6 * g_5 + p_6 * p_5 * g_4 + p_6 * p_5 * p_4 * c_4 = 4T + \max(g_6, p_6 * g_5, p_6 * p_5 * g_4, p_6 * p_5 * p_4 * c_4) \\ &= 4T + \max(2T, 4T, 5T, 4T + \max(p_6, p_5, p_4, c_4)) = 4T + \max(2T, 4T, 5T, 4T + \max(2T, 2T, 2T, 12T)) \\ &= 4T + \max(2T, 4T, 5T, 16T) = 4T + 16T = 20T \\ c_8 &= g_7 + p_7 * g_6 + p_7 * p_6 * g_5 + p_7 * p_6 * p_5 * g_4 + p_7 * p_6 * p_5 * p_4 * c_4 \\ &= 5T + \max(g_7, p_7 * g_6, p_7 * p_6 * g_5, p_7 * p_6 * p_5 * g_4, p_7 * p_6 * p_5 * p_4 * c_4) \\ &= 5T + \max(2T, 4T, 5T, 6T, 5T + \max(p_7, p_6, p_5, p_4, c_4)) \\ &= 5T + \max(2T, 4T, 5T, 6T, 5T + \max(2T, 2T, 2T, 12T)) \\ &= 5T + \max(2T, 4T, 5T, 6T, 17T) = 5T + 17T = 22T \end{aligned}$$

$$\text{Sum}_4 = 3T + c_4 = 3T + 12T = 15T$$

$$\text{Sum}_5 = 3T + c_5 = 3T + 16T = 19T$$

$$\text{Sum}_6 = 3T + c_6 = 3T + 18T = 21T$$

$$\text{Sum}_7 = 3T + c_7 = 3T + 20T = 23T$$

→ The delay time of  $p_i$  and  $g_i$  is overlapped since  $p_i$  and  $g_i$  are already available when the  $c_4$  arrives at 12T.

This delay overlap is applied to the **rest** of CLAs:

$$c(i+4) = c_i + 10T$$

$$\text{Sum}(i+3, i) = c_i + 11T$$

$$\text{CLA4bit}_{11,8}: \quad c_{12} = c_8 + 10T = 22T + 10T = 32T, \quad \text{Sum}_{11,8} = c_8 + 11T = 22T + 11T = 33T$$

$$\text{CLA4bit}_{15,12}: \quad c_{16} = c_{12} + 10T = 32T + 10T = 42T, \quad \text{Sum}_{15,12} = c_{12} + 11T = 32T + 11T = 43T$$

...

$$\text{CLA4bit}_{63,60}: \quad c_{64} = c_{60} + 10T = 152T + 10T = 162T, \quad \text{Sum}_{63,60} = c_{60} + 11T = 152T + 11T = 163T$$

c. 64bit ripple carry adder using **16 bit hierarchical carry-lookahead adder**:  $c_{64} = 49T$ ,  $\text{Sum} = 58T$

**HCLA16bit<sub>15,0</sub>:**  $c_{16} = 19T$ ,  $\text{Sum} = 28T$

$p_i = a * b = 2T$ ,  $g_i = a \text{ xor } b = 2T$  from each one bit adder

CLU-1level generates  $G_i$  and  $P_i$ .

$$G = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0 = 4T + \max(2T, 4T, 5T, 6T) = 10T$$

$$P = p_0 * p_1 * p_2 * p_3 = 4T + \max(2T, 2T, 2T, 2T) = 6T$$

$$G_0 = G_1 = G_2 = G_3 = 10T \text{ and } P_0 = P_1 = P_2 = P_3 = 6T$$

CLU-2level generates  $c_4, c_8, c_{12}, c_{16}$

The notation of CLU-2lev is same as 1-level CLU:  $g_i = G_i$ ,  $p_i = P_i$

$$c_4 = g_0 + p_0 * c_0 = 2T + \max(g_0, 2T + \max(p_0, c_0)) = 2T + \max(10T, 2T + 6T) = 2T + 10T = 12T$$

$$c_8 = g_1 + p_1 * g_0 + p_1 * p_0 * c_0 = 3T + \max(g_1, p_1 * g_0, p_1 * p_0 * c_0) = 3T + \max(10T, 12T, 3T + 6T) = 3T + 12T = 15T$$

$$c_{12} = g_2 + p_2 * g_1 + p_2 * p_1 * g_0 + p_2 * p_1 * p_0 * c_0 = 4T + \max(g_2, p_2 * g_1, p_2 * p_1 * g_0, p_2 * p_1 * p_0 * c_0)$$

$$\begin{aligned}
&= 4T + \max(10T, 12T, 13T, 4T+6T) = 4T+13T = 17T \\
c16 &= g3 + p3*g2 + p3*p2*g1 + p3*p2*p1*g0 + p3*p2*p1*p0*c0 \\
&= 5T + \max(g3, p3*g2, p3*p2*g1, p3*p2*p1*g0, p3*p2*p1*p0*c0) \\
&= 5T + \max(10T, 12T, 13T, 14T, 5T+6T) = 5T+14T = 19T
\end{aligned}$$

From solution b:

$$\text{Sum}(i+3, i) = ci + 11T$$

CLA4bit<sub>3,0</sub>: ...

$$\text{CLA4bit}_{7,4}: \text{Sum}_{7,4} = c4 + 11T = 12T + 11T = 23T$$

$$\text{CLA4bit}_{11,8}: \text{Sum}_{11,8} = c8 + 11T = 15T + 11T = 26T$$

$$\text{CLA4bit}_{15,12}: \text{Sum}_{15,12} = c12 + 11T = 17T + 11T = 28T$$

$$\text{HCLA16bit}_{31,16}: c32 = 29T, \text{Sum}_{31,16} = 38T$$

CLU-2level generates c20, c24, c28, c32

The notation of CLU-2lev is same as 1-level CLU:  $gi=Gi$ ,  $pi=Pi$ ,  $c0=c16$  (19T)

$$c20 = g0 + p0*c16 = 2T + \max(g0, 2T + \max(p0, c0)) = 2T + \max(10T, 2T + \max(6T, 19T))$$

$$= 2T + \max(10T, \max(8T, 21T)) = 2T + 21T = 23T$$

$$c24 = g1 + p1*g0 + p1*p0*c0 = 3T + \max(g1, p1*g0, p1*p0*c0) = 3T + \max(10T, 12T, 3T + \max(p1, p0, c0))$$

$$= 3T + \max(10T, 12T, 3T + \max(6T, 6T, 19T)) = 3T + \max(10T, 12T, 22T) = 25T$$

$$c28 = g2 + p2*g1 + p2*p1*g0 + p2*p1*p0*c0 = 4T + \max(g2, p2*g1, p2*p1*g0, 4T + \max(p2, p1, p0, c0))$$

$$= 4T + \max(10T, 12T, 13T, 4T + \max(6T, 6T, 6T, 19T)) = 4T + \max(10T, 12T, 13T, 23T) = 4T + 23T = 27T$$

$$c32 = g3 + p3*g2 + p3*p2*g1 + p3*p2*p1*g0 + p3*p2*p1*p0*c0$$

$$= 5T + \max(g3, p3*g2, p3*p2*g1, p3*p2*p1*g0, p3*p2*p1*p0*c0)$$

$$= 5T + \max(10T, 12T, 13T, 14T, 5T + \max(p3, p2, p1, p0, c0))$$

$$= 5T + \max(10T, 12T, 13T, 14T, 5T + \max(6T, 6T, 6T, 6T, 19T)) = 5T + 24T = 29T$$

$$\text{CLA4bit}_{19,16}: \text{Sum}_{19,16} = c16 + 11T = 19T + 11T = 30T$$

$$\text{CLA4bit}_{23,20}: \text{Sum}_{23,20} = c20 + 11T = 23T + 11T = 34T$$

$$\text{CLA4bit}_{27,24}: \text{Sum}_{27,24} = c24 + 11T = 25T + 11T = 36T$$

$$\text{CLA4bit}_{31,28}: \text{Sum}_{31,28} = c28 + 11T = 27T + 11T = 38T$$

→ The delay time of  $Pi$  and  $Gi$  is overlapped since  $Pi$  and  $Gi$  are already available when the  $c16$  arrives at 19T.

This delay overlap is applied to the rest of HCLAs:

$$c(i+16) = ci + 10T$$

$$\text{Sum}(i+15, i) = c(i+12) + 11T = ci + 8T + 11T = ci + 19T$$

$$\text{HCLA16bit}_{47,32}: c48 = c32 + 10T = 29T + 10T = 39T, \text{Sum}_{47,32} = c32 + 19T = 29T + 19T = 48T$$

$$\text{HCLA16bit}_{63,48}: c64 = c48 + 10T = 39T + 10T = 49T, \text{Sum}_{63,48} = c48 + 19T = 39T + 19T = 58T$$

d. 64bit **three-level** carry-lookahead adder:  $c_{64}=27T$ ,  $\text{Sum}=44T$

$p_i = a * b = 2T$ ,  $g_i = a \text{ xor } b = 2T$  from each one bit adder

CLU-1level generates  $G_i$  and  $P_i$ .

$$G = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0 = 4T + \max(2T, 4T, 5T, 6T) = 10T$$

$$P = p_0 * p_1 * p_2 * p_3 = 4T + \max(2T, 2T, 2T, 2T) = 6T$$

$$G_0=G_1=G_2=G_3=10T \text{ and } P_0=P_1=P_2=P_3=6T$$

CLU-2level generates  $G_{i\_2lev}$  and  $P_{i\_2lev}$

$$G_{\_2lev} = G_3 + G_3 * G_2 + P_3 * P_2 * G_1 + P_3 * P_2 * P_1 * G_0 = 4T + \max(10T, 12T, 13T, 14T) = 4T + 14T = 18T$$

$$P_{\_2lev} = P_0 * P_1 * P_2 * P_3 = 4T + \max(6T, 6T, 6T, 6T) = 10T$$

$$G_{0\_2lev}=G_{1\_2lev}=G_{2\_2lev}=G_{3\_2lev}=18T \text{ and } P_{0\_2lev}=P_{1\_2lev}=P_{2\_2lev}=P_{3\_2lev}=10T$$

CLU-3lev generates  $c_{16}$ ,  $c_{32}$ ,  $c_{48}$ ,  $c_{64}$

The notation is same as 1-level CLU:  $g_i=G_{i\_2lev}$ ,  $p_i=P_{i\_2lev}$

$$c_{16} = g_0 + p_0 * c_0 = 2T + \max(g_0, 2T + \max(p_0, c_0)) = 2T + \max(18T, 2T + \max(10T, 0T)) = 2T + 18T = 20T$$

$$c_{32} = g_1 + p_1 * g_0 + p_1 * p_0 * c_0 = 3T + \max(g_1, p_1 * g_0, p_1 * p_0 * c_0) = 3T + \max(18T, 20T, 13T) = 3T + 20T = 23T$$

$$c_{48} = g_2 + p_2 * g_1 + p_2 * p_1 * g_0 + p_2 * p_1 * p_0 * c_0 = 4T + \max(g_2, p_2 * g_1, p_2 * p_1 * g_0, p_2 * p_1 * p_0 * c_0) \\ = 4T + \max(18T, 20T, 21T, 14T) = 25T$$

$$c_{64} = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0 + p_3 * p_2 * p_1 * p_0 * c_0 \\ = 5T + \max(g_3, p_3 * g_2, p_3 * p_2 * g_1, p_3 * p_2 * p_1 * g_0, p_3 * p_2 * p_1 * p_0 * c_0) \\ = 5T + \max(18T, 20T, 21T, 22T, 15T) = 5T + 22T = 27T$$

From solution c:

$$\text{Sum}(i+15, i) = c_i + 19T$$

HCLA16bit<sub>15,0</sub>: ...

$$\text{HCLA16bit}_{31,16}: \text{Sum}_{31,16} = c_{16} + 19T = 20T + 19T = 39T$$

$$\text{HCLA16bit}_{47,32}: \text{Sum}_{47,32} = c_{32} + 19T = 23T + 19T = 42T$$

$$\text{HCLA16bit}_{63,48}: \text{Sum}_{63,48} = c_{48} + 19T = 25T + 19T = 44T$$